

CSE 306

COMPUTER ARCHITECTURE SEASIONAL

Assignment 3 : 8-bit MIPS Design and Simulation

Section : A2

Group No : 03

Student ID:


1.1605051

2.1705040

3.1705042

4.1705048

5.1705054

 

Submission Date: 20.06.2021

Introduction

MIPS (Microprocessor without Interlocked Pipelined Stages) is a reduced instruction set computer (RISC) instruction set architecture (ISA). MIPS only takes register values as operands for arithmetic operations. MIPS has thirty-two 32-bit general-purpose registers (GPR). Register \$zero is hardwired to zero and writes to it are discarded. The program counter has 32 bits. Instructions are divided into three types: R, I and J. Every instruction starts with a 6-bit opcode. In addition to the opcode, R-type instructions specify three registers, a shift amount field, and a function field; I-type instructions specify two registers and a 16-bit immediate value; J-type instructions follow the opcode with a 26-bit jump target.

In this assignment, we designed an 8-bit processor that implements the MIPS instruction set. Here, each instruction takes 1 clock cycle to be executed. The length of the clock cycle is long enough to execute the longest instruction in the MIPS instruction set. The main components of our 8-bit processor are as follows: instruction memory, data memory, register file, ALU, and a control unit. To simulate our design, we needed to use an assembly code. Before starting the simulation, we converted the given assembly code into MIPS machine code and loaded the machine code into the instruction memory.

Problem Specification

In this assignment, we were required to implement an 8-bit processor that implements add, addi, sub, subi, and, andi, or, ori, sll, srl, nor, sw, lw, beq, bneq, j with the “FDNKLIMJEOPBGCHA” sequence of opcodes. Also, we were required to design push and pop operations in our MIPS design using a stack. Our MIPS instructions were 20-bits long with the following three formats.

- R-type

Opcode	Src Reg 1	Src Reg 2	Dst Reg	Shft Amnt
4-bits	4-bits	4-bits	4-bits	4-bits
- I-type


Opcode	Src Reg	Dst Reg	Address / Immediate
4-bits	4-bits	4-bits	8-bits
- J-type

Opcode	Target Jump Address	0	0
4-bits	8-bits	4-bits	4-bits


INSTRUCTION SET DESCRIPTION

Instruction ID	Category	Type	Instruction
A	Arithmetic	R	add
B	Arithmetic	I	addi
C	Arithmetic	R	sub
D	Arithmetic	I	subi
E	Logic	R	and
F	Logic	I	andi
G	Logic	R	or
H	Logic	I	ori
I	Logic	R	sll
J	Logic	R	srl
K	Logic	R	nor
L	Memory	I	sw
M	Memory	I	lw
N	Control-conditional	I	beq
O	Control-conditional	I	bneq
P	Control-unconditional	J	j


High Level Block Diagram

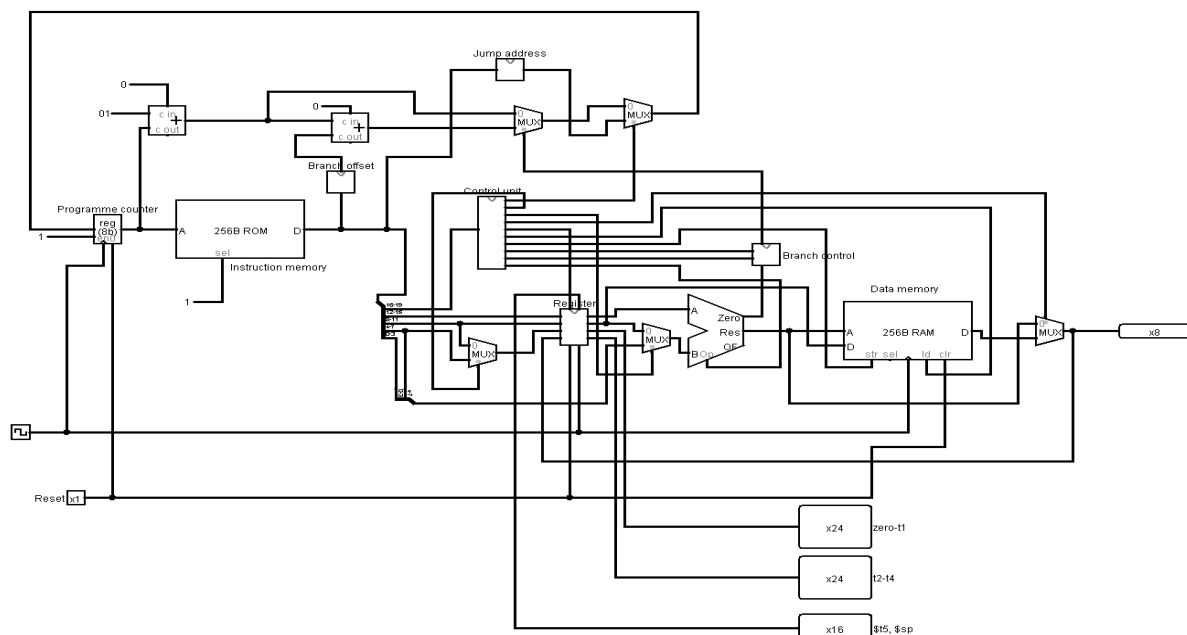


Instruction memory with PC

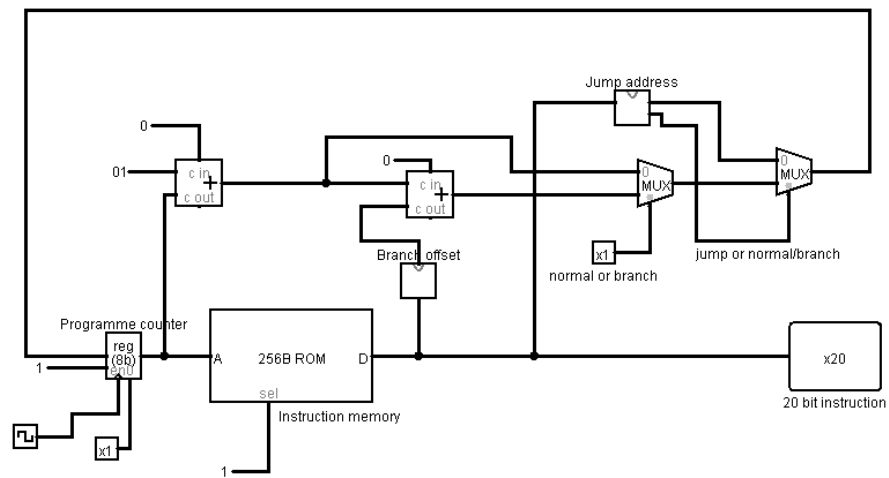


Register File

 


Register File Circuit

 


Control Unit

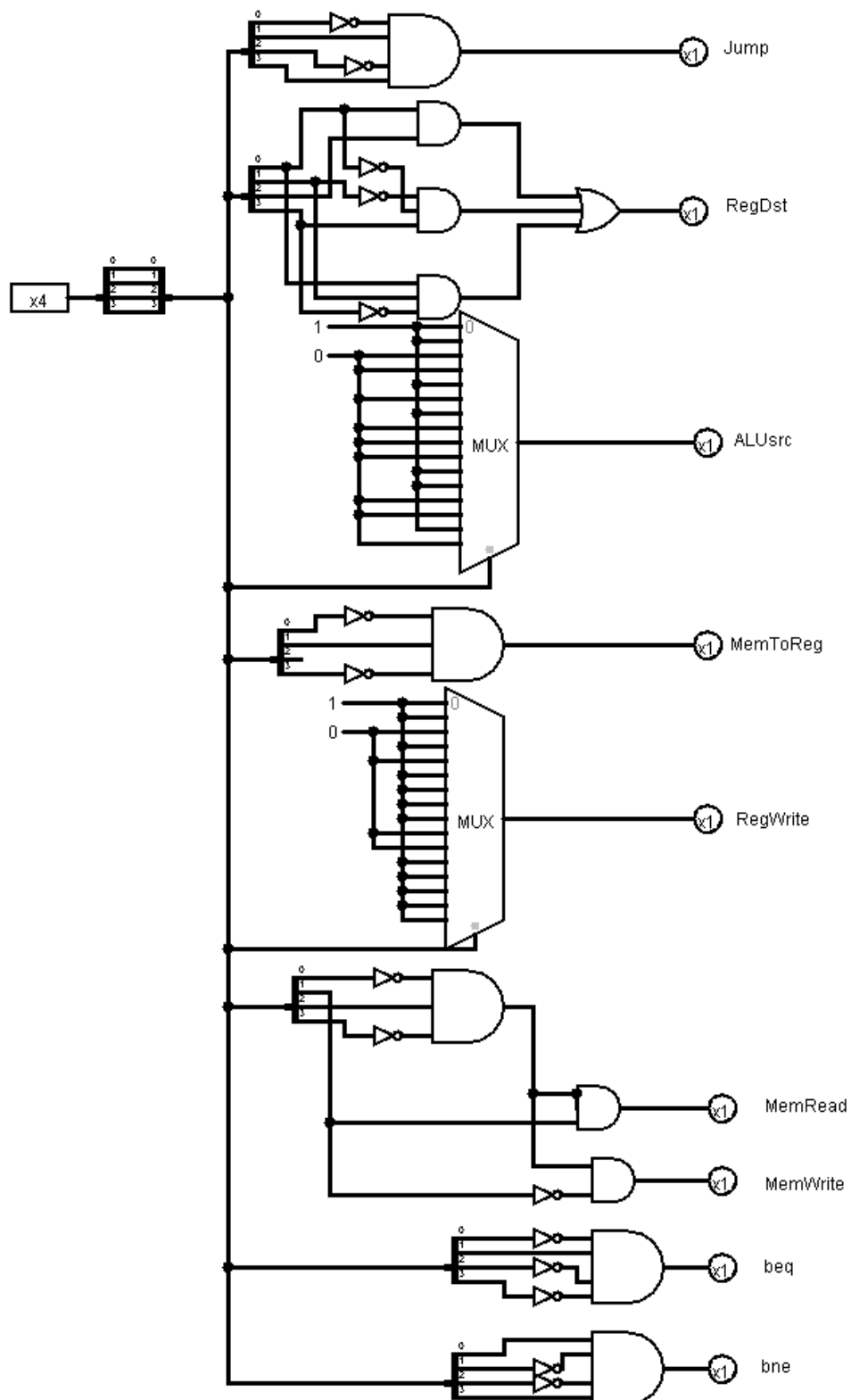


ALU Control Unit

 


Jump Address

 

Branch Selector

 

Branch Offset

 

Approach To Implement Push Pop

For implementing push instruction , we considered two cases –

case -01: push 0(\$t0)

corresponding assembly instructions ,

lw \$t5, 2(\$t0)

sw \$t5, 0(\$sp)

subi \$sp, \$sp, 1

case -02: push \$t0

corresponding assembly instructions ,

sw \$t0, 0(\$sp)

subi \$sp, \$sp, 1

To implement push instruction , we performed load, store and subtract immediate operations respectively.

Accordingly, we used store and add immediate operations for implementing pop instruction.

pop \$t0

lw \$t0, 0(\$sp)

addi \$sp, \$sp, 1

Required ICs And Components

IC Number	IC Type	Count
7408	quad 2 input AND gate	29
7432	quad 2 input OR gate	3
7404	hex NOT gate	19
74148	8*3 priority encoder	1
74138	3*8 decoder	1
7480	1 bit adder	8
74151	8*1 MUX	2
74150	16*1 MUX	2
	8-bit register	9
	ROM	1
	RAM	1

Simulator Used

Logisim-generic: 2.7.1

Discussion

In this assignment, we designed an 8-bit processor that implements the MIPS instruction set using AND gate, OR gate, NOT gate, Adder, Priority Encoder, Multiplexer, Decoder, Register and ROM. We counted the IC number according to the ICs available in the real world. For initializing stack pointer \$sp we have set a clock pulse. We used separate instruction and data memories as we can not access both the data and instruction memory at the same time. Memory is actually divided between instruction and data in a single-cycle machine as memory can only be accessed once per cycle.